
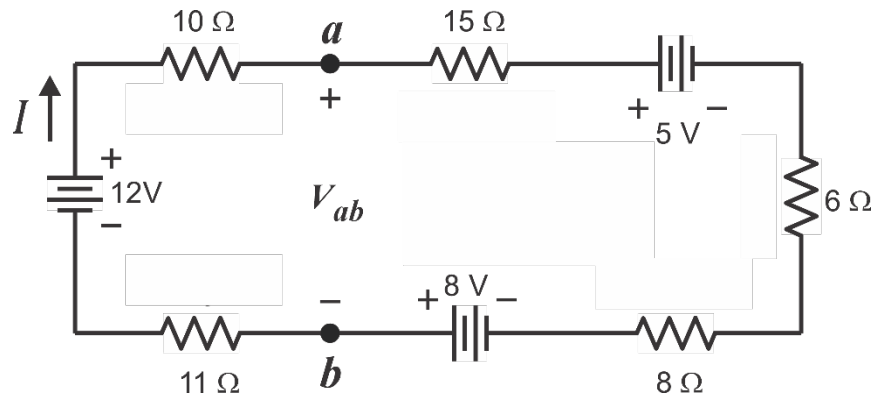


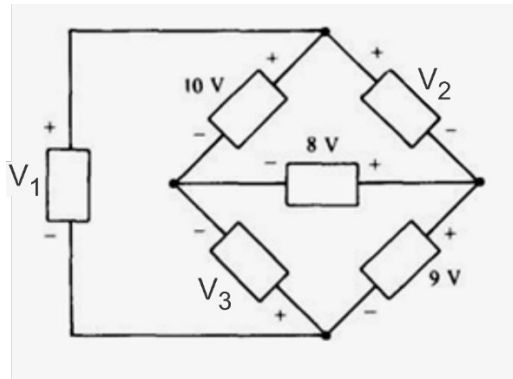
1. **KVL and Ohm's Law:** Find the current, I , and V_{ab} in the following circuit. V_{ab} is the voltage drop across nodes **a-b**.



2. **KVL:** Find the unknown voltages, V_1 , V_2 , and V_3 , in the following circuit.




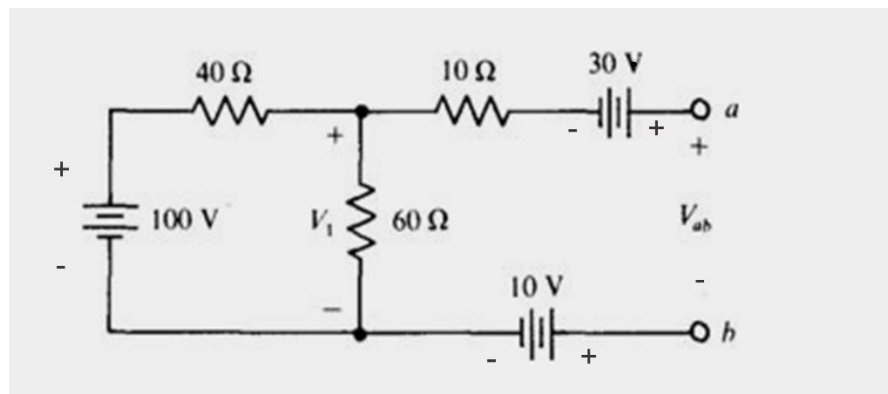3. **KVL and Ohm's Law:** Find the voltage, V_{ab} , across the open circuit (open terminals on the right) in the following circuit. Hint: current only flows in the loop on the left.



Continue to next page

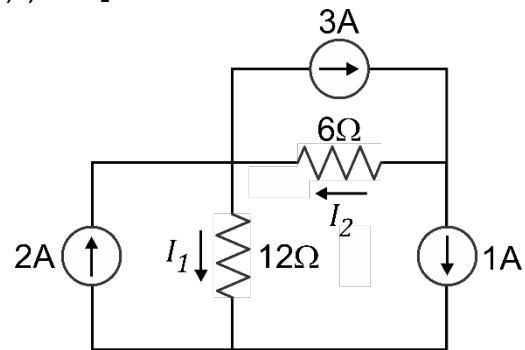4. **KCL:** Using KCL, find the unknown currents, I_1 and I_2 .



5. **KCL and Ohm's Law:** find the unknown currents I_1 , I_2 and I_3 .

