

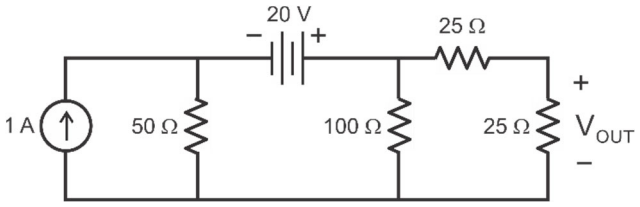
1. **Nodal Analysis using a Supernode:**
   a) Clearly **identify** all the nodes including the "Supernode" (draw circle around Supernode) .
   b) Find V_{OUT}



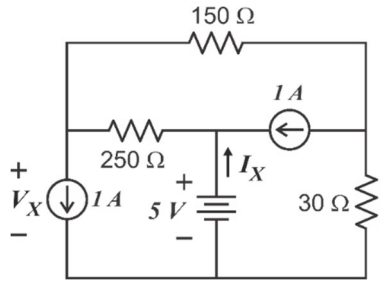2. **Mesh Analysis using a Supermesh:**
   a) For the following circuit with two independent current sources and one independent voltage source, clearly identify all the mesh currents including the Supermesh loop.
   b) Using Mesh Analysis, including the Supermesh, **find** all your unknown **mesh currents**. **Place the values on a table**.
   c) Find I_X and V_X



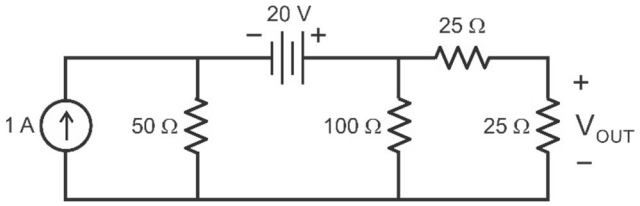3. **Superposition:**
   Using the circuit in problem 1, find V_{OUT} using Superposition.



4. **Superposition**
   Find V_{OUT} using Superposition, noting the "dependent current source".

